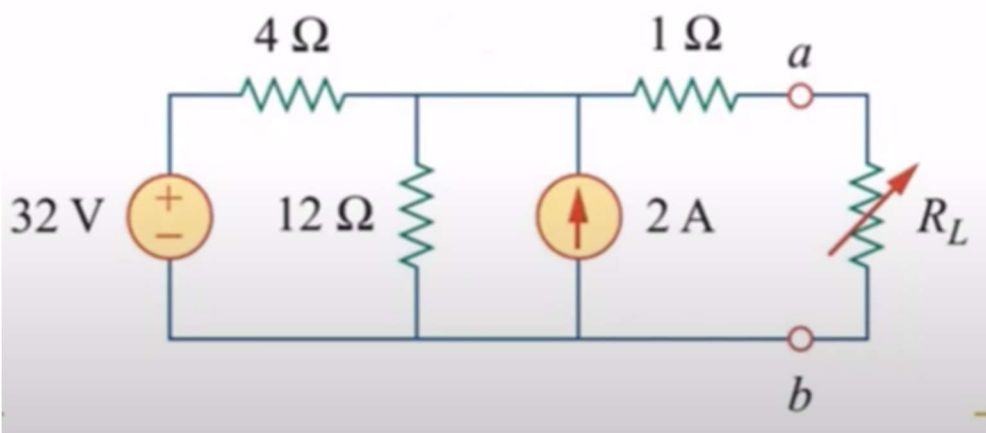


Steps to find Thevenin's equivalent circuit

1. Identify the load terminals.
2. Remove the load resistance from the circuit (if its is connected)
3. Find the equivalent resistance (R_{Th}) across the load terminal by replacing independent voltage source by short circuit and independent current source by open circuit
4. Find the open circuit voltage (V_{Th}) using any of the circuit analysis techniques (mostly mesh/node methods)
5. Draw the Thevenin's equivalent circuit

Problem:




2. First Remove R_{load}

3.

Voltage source \rightarrow short circuit


Current source \rightarrow open circuit

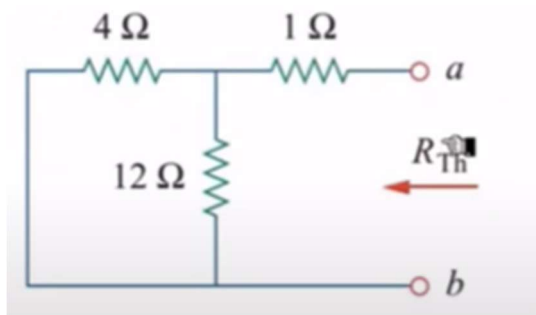

Calculate R_{th}

$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4\ \Omega$$

4. Find Voltage V_{th}

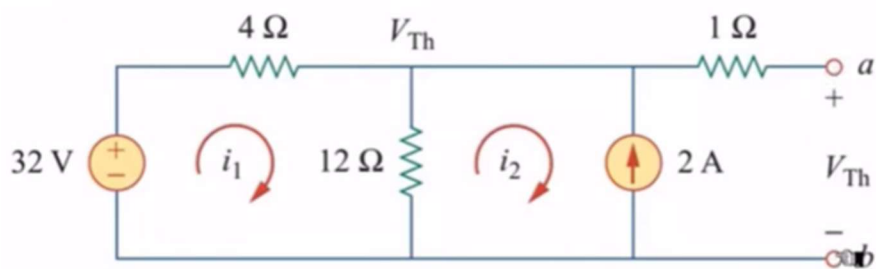


$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2\text{ A}$$

Solving for i_1 , we get $i_1 = 0.5\text{ A}$. Thus,

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30\text{ V}$$

5. Place R_{load} back, and determine current:

Thevenin's Equivalent Circuit

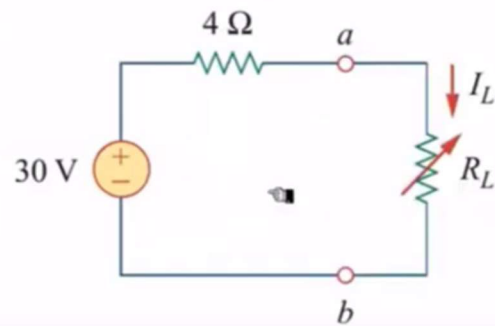

$$I_L = \frac{V_{\text{Th}}}{R_{\text{Th}} + R_L} = \frac{30}{4 + R_L}$$